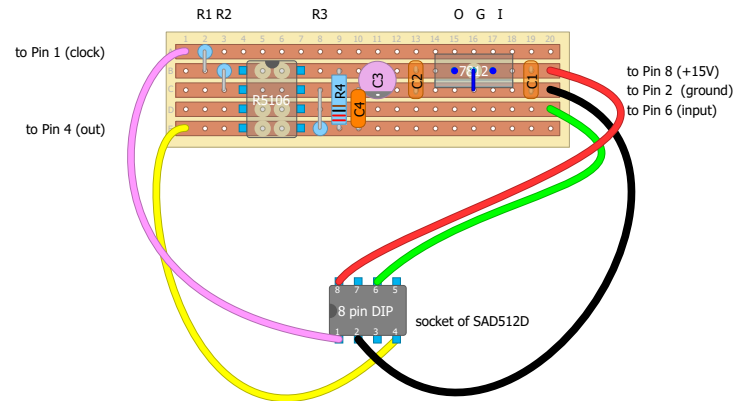


Daughterboard to replace SAD512D with R5106 in DOD 670



Vero Board	qty 1
7812	7812 Regulator
8 pin DIP	8 pin DIP socket of SAD512D
C1, C2, C4	0.1uF 16V
C3	22uF 16V
R1, R4	2200Ω 0.25W
R2, R3	10K 0.25W
R5106	R5106 IC in 8 pin DIP socket